

VHDL Tehtävä 1 : JK-Kiikku – toteutettu IF:llä**Koodi:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity JK_kiikku2 is
  Port ( J : in std_logic;
        K : in std_logic;
        CLK : in std_logic;
        Reset : in std_logic;
        Q : out std_logic;
        Q_not : out std_logic);
end JK_kiikku2;

architecture Behavioral of JK_kiikku2 is

begin

process(J,K,CLK,Reset)

variable MP_Q : std_logic;
variable MP_Q_not : std_logic;

begin

if (Reset = '1') then
  MP_Q := '0';
  MP_Q_not := '1';
  Q <= '0';
  Q_not <= '1';

elsif (CLK'event and CLK = '1') then
  if (J = '0' and K = '0') then
    Q <= MP_Q;
    Q_not <= MP_Q_not;
  elsif (J = '0' and K = '1') then
    MP_Q := '0';
    MP_Q_not := '1';
    Q <= MP_Q;
    Q_not <= MP_Q_not;
  elsif (J = '1' and K = '0') then
    MP_Q := '1';
    MP_Q_not := '0';
    Q <= MP_Q;
```


```
        Q_not <= MP_Q_not;
    elsif (J = '1' and K = '1') then
        MP_Q := not MP_Q;
        MP_Q_not := not MP_Q_not;
        Q <= MP_Q;
        Q_not <= MP_Q_not;
    end if;
end if;

end process;

end Behavioral;
```

end Behavioral;

Simulointi:

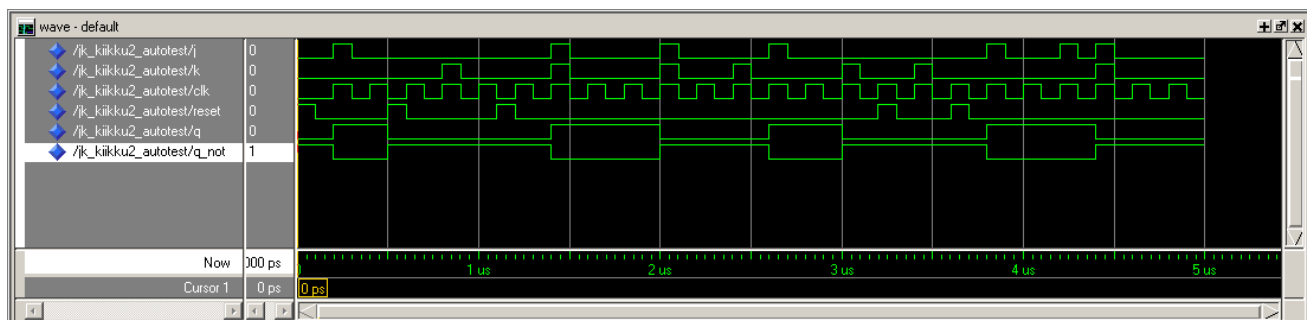

VHDL Tehtävä 1 : JK-Kiikku – toteutettu WHEN:llä**Koodi:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity JK_kiikku3 is
  Port ( J : in std_logic;
        K : in std_logic;
        CLK : in std_logic;
        Reset : in std_logic;
        Q : out std_logic;
        Q_not : out std_logic);
end JK_kiikku3;

architecture Behavioral of JK_kiikku3 is

begin

process(J,K,CLK,Reset)

variable MP_Q : std_logic;
variable MP_Q_not : std_logic;
variable sel : std_logic_vector(1 downto 0);

begin

sel := J&K;

if (Reset = '1') then
  MP_Q := '0';
  MP_Q_not := '1';
  Q <= '0';
  Q_not <= '1';


elsif (CLK'event and CLK = '1') then
  case (sel) is
    when "00" =>
      Q <= MP_Q;
      Q_not <= MP_Q_not;
    when "01" =>
      MP_Q := '0';
      MP_Q_not := '1';
      Q <= MP_Q;
      Q_not <= MP_Q_not;
```

```
when "10" =>
  MP_Q := '1';
  MP_Q_not := '0';
  Q <= MP_Q;
  Q_not <= MP_Q_not;
when "11" =>
  MP_Q := not MP_Q;
  MP_Q_not := not MP_Q_not;
  Q <= MP_Q;
  Q_not <= MP_Q_not;
when others =>
end case;
end if;

end process;
```

end Behavioral;

Simulointi:

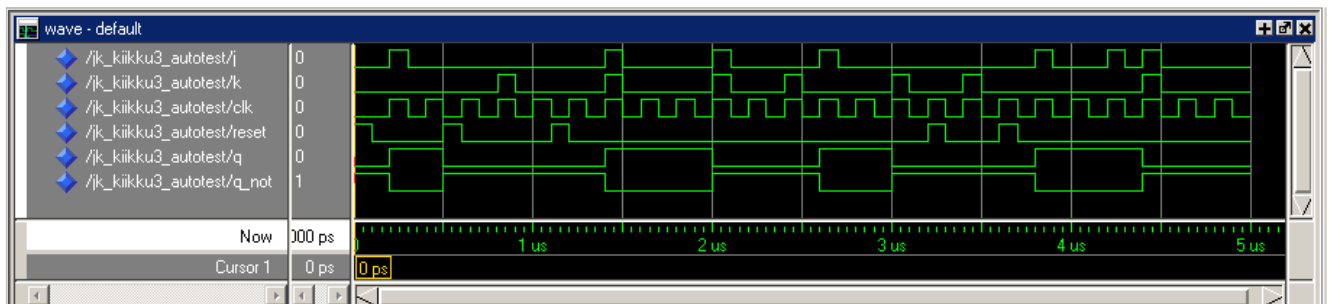

VHDL Tehtävä 2 : My_and_or

Koodi:

my_and-behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity My_and is
  Port ( I1 : in std_logic;
        I2 : in std_logic;
        O1 : out std_logic);
end My_and;
```

```
architecture Behavioral of My_and is
```

```
begin
```

```
    O1 <= I1 and I2;
```

```
end Behavioral;
```

my_or-behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity my_or is
  Port ( I1 : in std_logic;
        I2 : in std_logic;
        O1 : out std_logic);
end my_or;
```

```
architecture Behavioral of my_or is
```

```
begin
```

```
    O1 <= I1 or I2;
```

```
end Behavioral;
```

my_and_or-behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity my_and_or is
    Port ( A : in std_logic;
          B : in std_logic;
          C : in std_logic;
          D : in std_logic;
          Z : out std_logic);
end my_and_or;


architecture Behavioral of my_and_or is

    COMPONENT my_and
        Port ( I1 : in std_logic;
              I2 : in std_logic;
              O1 : out std_logic);
    end component;

    COMPONENT my_or is
        Port ( I1 : in std_logic;
              I2 : in std_logic;
              O1 : out std_logic);
    end component;

    signal SIG1 : std_logic;
    signal SIG2 : std_logic;

begin
    my_and1 : my_and port map ( I1=>A, I2=>B, O1=>SIG1 );
    my_and2 : my_and port map ( I1=>C, I2=>D, O1=>SIG2 );
    my_or1 : my_or port map ( I1=>SIG1, I2=>SIG2, O1=>Z );
end Behavioral;
```

 Simulointi:

VHDL Tehtävä 3 : PWM-modulaattori

Koodi:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity PWM is
  Port ( clock : in std_logic;
        ref : in std_logic_vector(7 downto 0);
        enable_PWM : in std_logic;
        reset_PWM : in std_logic;
        PWM_out : out std_logic
        );
end PWM;

architecture Behavioral of PWM is

  signal count : std_logic_vector(7 downto 0);

begin

  process (clock, reset_PWM, enable_PWM)
  begin

    if reset_PWM = '1' or enable_PWM = '0' then
      count <= "00000000";
      PWM_out <= '0';

    elsif clock='0' and clock'event and enable_PWM='1' and reset_PWM = '0' then

      if count < "11111111" then

        count <= count + '1';

        if count > ref then
          PWM_out <= '0';
        else
          PWM_out <= '1';
        end if;

      else
        count <= "00000000";
      end if;

    end if;


  end process;

end Behavioral;
```


```
end if;  
end process;  
end Behavioral;
```

Simulointi:


Lähtö 0% -ohjauksella

 

Lähtö 50% -ohjauksella

 

Lähtö 100% -ohjauksella

 

VHDL Tehtävä : FOR LOOP and

Koodi:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity forluoppiandi is
  Port ( A : in std_logic_vector(7 downto 0);
        B : in std_logic_vector(7 downto 0);
        Z : out std_logic_vector(7 downto 0));
end forluoppiandi;

architecture Behavioral of forluoppiandi is

begin
  process (A,B)
  begin
    for i in 7 downto 0 loop
      Z(i) <= A(i) and B(i);
    end loop;
  end process;
end Behavioral;
```

Teknologiatoteutus:

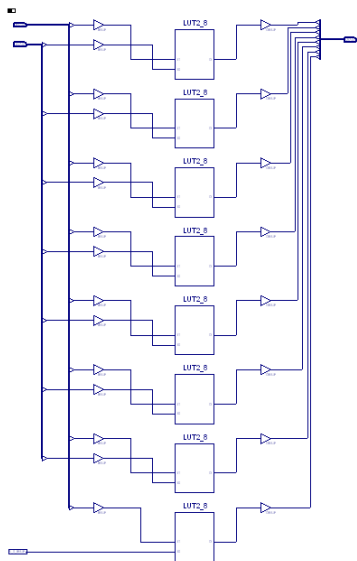

VHDL Tehtävä : FOR LOOP laskuri**Koodi:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity forluuppilaskuri is
  Port ( out1 : out std_logic;
        clk : in std_logic;
        aa: out integer;
        reset : in std_logic);
end forluuppilaskuri;

architecture Behavioral of forluuppilaskuri is

begin

process (clk)
variable laskuri : integer;

begin

if reset = '1' then
  laskuri := 0;
  aa <= 0;


elsif clk='1' and clk'event then

      for i in 19 downto 0 loop
        laskuri := laskuri + 1;
        if laskuri > 100 then
          out1 <= '0';
        else
          out1 <= '1';
        end if;
        aa <=laskuri;
      end loop;

end if;
end process;

end Behavioral;
```

Teknologiatoteutus:

 

41 sivua pelkkää p*skaa generoitu for-loopin ansiosta. Yllä oleva kuva esittää yhden sivun sisältöä.

VHDL Tehtävä : Generic ja Generate

Koodi:

generic_generate-behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity generic_generate is
    generic (cycles: positive:=10);
    Port(D,clr,clk : in bit;
          q : out bit);
end generic_generate;

architecture Behavioral of generic_generate is
    component dff is
        Port(D,clr,clk : in bit;
              q : out bit);
    end component;

    signal s :bit_vEctor(cycles - 1 downto 1);

    begin

    cycleEQ1:if cycles = 1 generate
    d1: dff port map (D,clr,clk,q);
    end generate cycleEQ1;

    cycleGT1: if cycles > 1 generate
    first:dff port map (D,clr,clk,s(1));
    inTheMiddle:For i in 2 to cycles-1 generate
    di: dff port map (s(i-1),clr,clk,s(i));
    end generate;

    last: dff port map (s(cycles-1),clr,clk,q);
    end generate cycleGT1;
end Behavioral;
```

dff-behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dff is
  Port ( D : in std_logic;
        clr : in std_logic;
        clk : in std_logic;
        q : out std_logic);
end dff;

architecture Behavioral of dff is

begin

  process (D,clr,clk)
  begin
    if (clr='1') then
      q <= '0';

    elsif (clk'event and clk='1' and clr='0') then
      q <= D;
    end if;

  end process;

end Behavioral;
```